



DR. MITHUN BHOWAL

PHN NO: 9874577633

9038473239

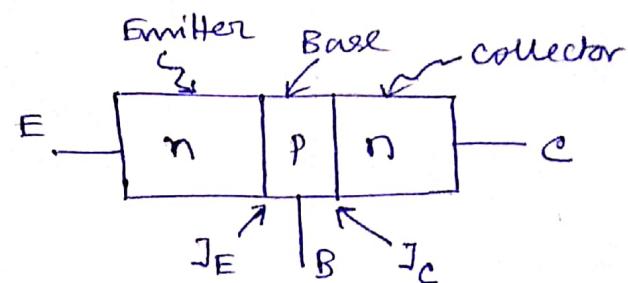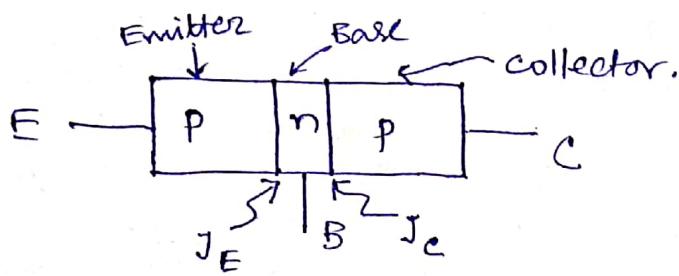
## BIPOLAR JUNCTION TRANSISTOR

A BJT is a three layer, two junction semiconductor device. It is formed by sandwiching a p-type or an n-type material between two opposite types of material forming either an n-p-n and p-n-p transistors. The three regions of a transistor are called emitter, base and collector. p-n-p and n-p-n transistors are schematically shown in fig. The middle portion of the transistor is called the base, and the two end portions are known as emitter and



the collector. The emitter-base junction is usually referred to as the emitter junction ( $J_E$ ) and the collector-base junction is referred to as collector junction ( $J_C$ ). Since both the majority and minority carriers are involved in a junction transistor, this device is termed the bipolar junction transistor (BJT).

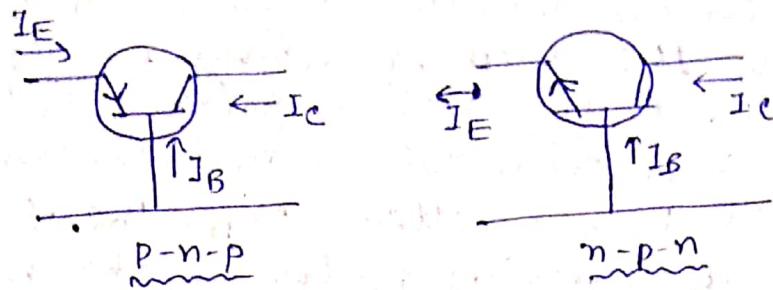In the normal transistor operation, emitter-base junction is forward biased and the collector-base junction is reverse biased. The circuit symbols for the p-n-p and n-p-n transistor is shown in fig. The arrow on the emitter specifies the direction of the current when emitter-base junction is forward biased.




Therefore, the current enters the transistor through the emitter terminal for a p-n-p transistor and leaves the transistor through the emitter terminal for an n-p-n transistor.

In transistors, the emitter layer is heavily doped and the collector only lightly doped. The doping of base layer is also made considerably lower than that of the outer layers. For normal operation emitter-base junction is forward biased and collector-base junction is reverse biased. The emitter (in p-n-p transistor) injects holes into base and these holes are finally collected by the collector. Since the E-B junction is forward biased its dynamic resistance is small and since the C-B junction is reverse biased its dynamic resistance is large. Due to transistor action it is found that an almost same current passes from a low resistor input circuit to a high resistor output circuit. The term transistor has been derived from the words 'transfer resistor'.
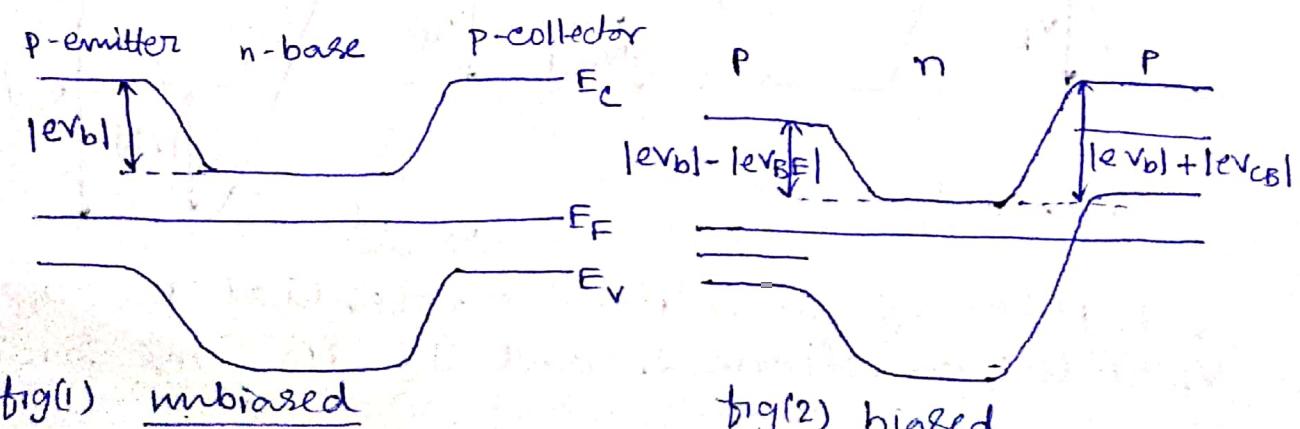
### Energy band diagram of a Transistor :-


In fig (1) shows the energy band diagram of an unbiased transistor with completely symmetric p-n junctions, where  $V_b$  is the



fig(1) unbiased

fig(2) biased


(3) intrinsic potential barrier at the two junctions. In fig(2) shows the corresponding energy band diagram with E-B junction forward biased by a voltage  $V_{EB}$  and collector base junction reverse biased by a voltage  $V_{CB}$ . The forward biasing of E-B junction reduces the intrinsic energy barrier  $|V_{EB}|$  to the  $|V_{EB}| - |V_{EBB}|$  and the reverse biasing of C-B junction increases the energy barrier to  $|V_{CB}| + |V_{CBI}|$ . Similar diagram for n-p-n transistors.

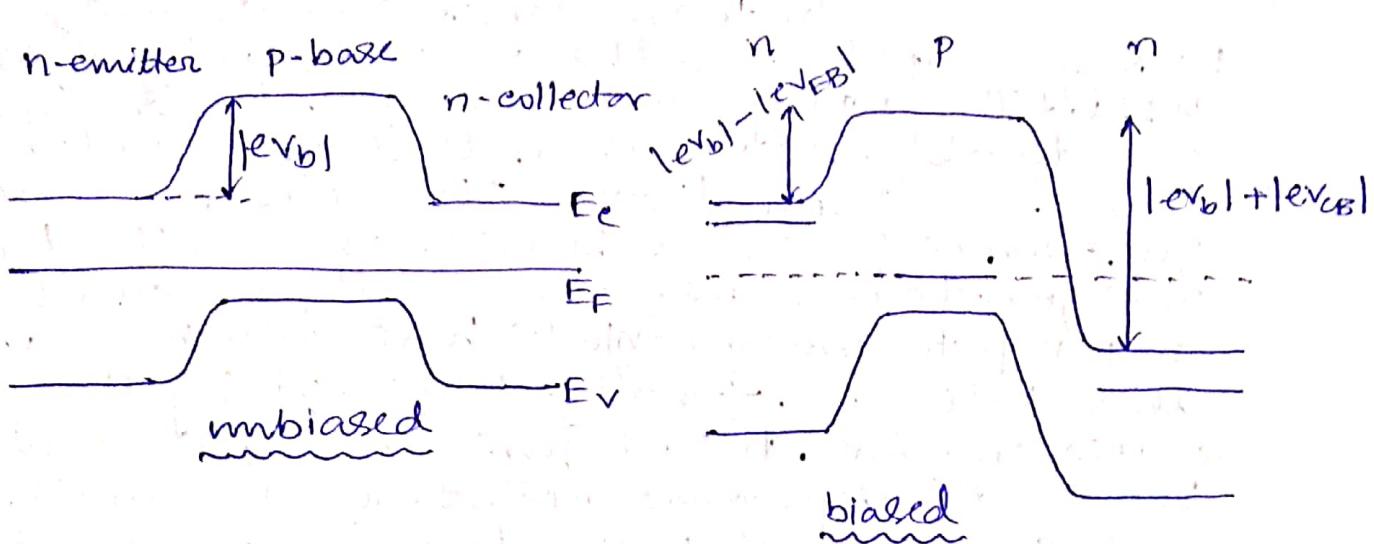

### Transistor operation and current component:-
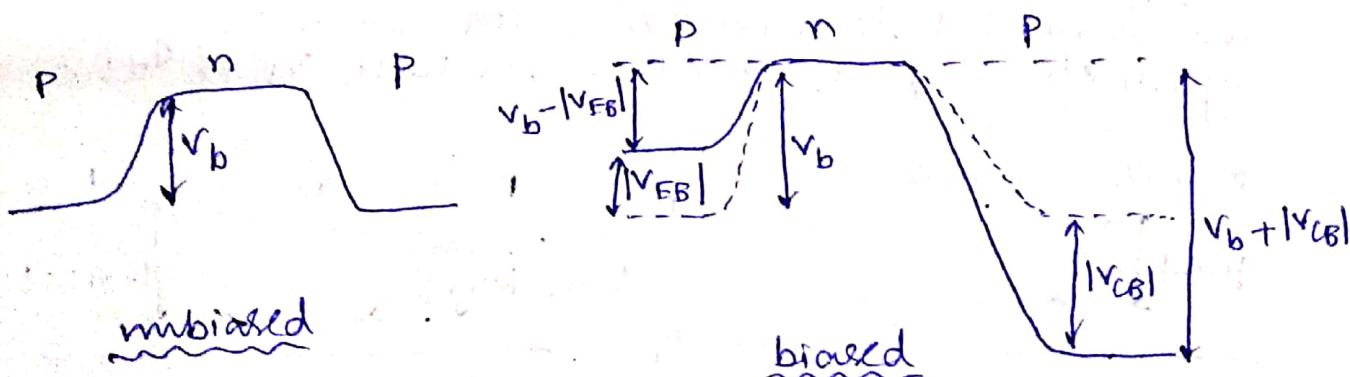
#### for P-n-p transistor:-


We consider a p-n-p transistor with its E-B junction forward biased and C-B junction reverse biased. In the absence of any external bias all the currents through the transistor must be zero. In fig 8 shows the potential distribution in an unbiased p-n-p transistor.



and there is an intrinsic potential barrier  $V_b$  at the junctions  $J_E$  and  $J_C$ . Now the forward

biasing voltage  $V_{EB}$  reduces the emitter base potential barrier to  $V_b - |V_{EB}|$  whereas the reverse biasing voltage  $V_{CB}$  increases the potential barrier across collector to  $V_b + |V_{CB}|$

The lowering of emitter junction barrier permits injection of holes from emitter to base and injection of electrons from base to emitter. These two flows constitute the emitter current as  $I_E = I_{PE} + I_{nE}$  where  $I_{PE}$  is due to holes moving from emitter to base and  $I_{nE}$  is due to electrons going from base to emitter. As doping of emitter region is much higher than that of the base. So  $I_{PE} \gg I_{nE}$

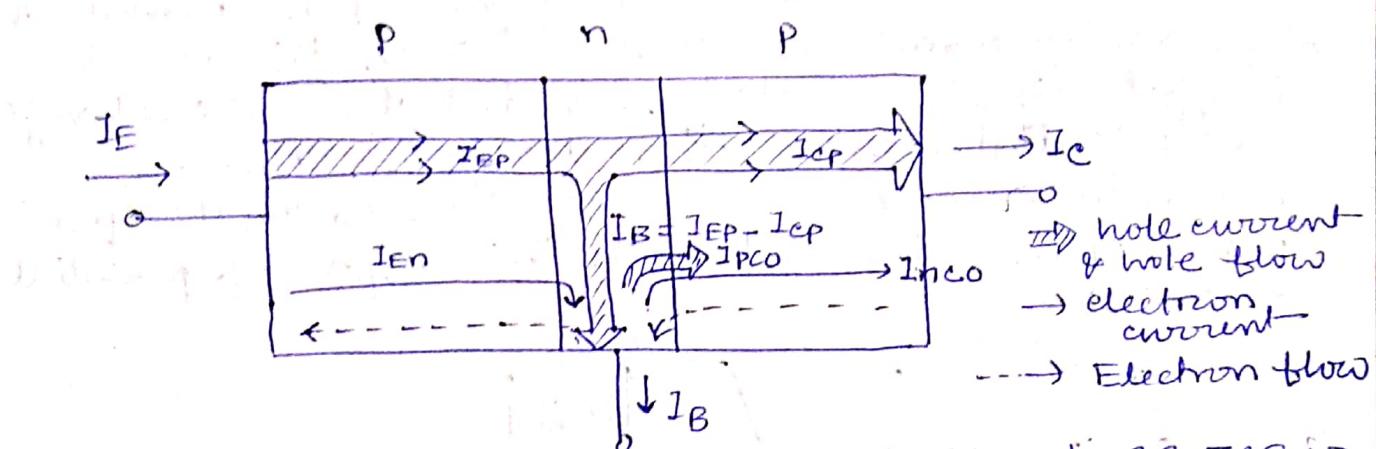

The injected holes diffuse through the base region towards the collector junction while diffusing through the base a few of the injected holes (typically 1-3%) are lost due to recombination with majority electrons in the base. The hole reaching the collector junction fall down the potential barrier and are immediately collected by the collector. This gives rise to the component  $I_{PC}$  of the collector current.  $I_{PC}$  is slightly smaller than  $I_{PE}$  and the difference ( $I_{PE} - I_{PC}$ ) constitutes a part of the base current. Since the collector junction is reverse biased there is a small collector current even with emitter open. This  $I_{C0}$  current consists of two components:  $I_{nCO}$  due to minority electrons flowing from p-side to n-side across base collector junction  $I_C$  and  $I_{PC0}$  due to minority

⑤ holes moving from n-side do p-side across  $J_c$ .  
 The resultant  $I_{nco} + I_{pco} = I_{co} = \text{reverse saturation current}$ .

We can now express the terminal currents in term of the various current component describe above:-

$$I_E = I_{EP} + I_{En}$$

$$I_C = I_{pct} + I_{net}$$

$$I_B = I_E - I_C$$


$$= (I_{EP} + I_{En}) - (I_{pct} + I_{net})$$

$$I_E = I_B + I_C$$


for n-p-n transistor :-

The operation of an n-p-n transistor is exactly same as above but with the roles played by the electrons and holes interchange.

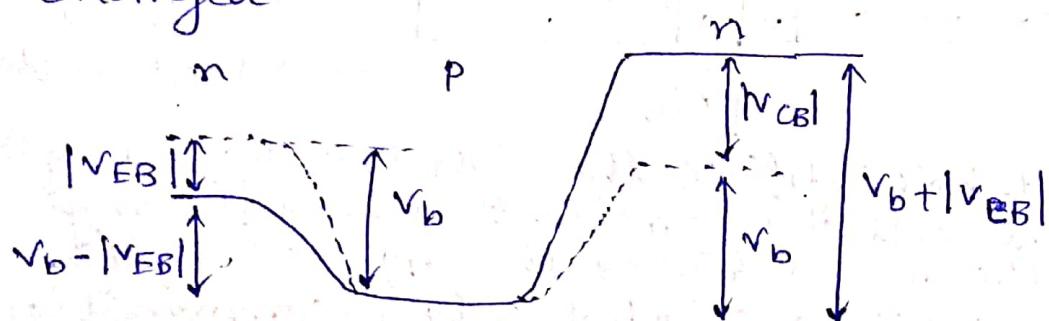The potential distribution diagram for an n-p-n transistor will be similar to that of a p-n-p transistor but with the sign of potential changed.



Here the majority electrons from emitter are injected into the base and majority holes from base are injected into emitter region. The two constitutes the emitter current as  $I_E = I_{nE} + I_{pE}$ . Since the doping of emitter region is much higher than that of the base,  $I_{nE} \gg I_{pE}$  and we have  $I_E \approx I_{nE}$ . The injected electrons diffuse through base towards the collector junction. A few of injected electrons are lost due to recombination with majority holes in the base. The electrons reaching the

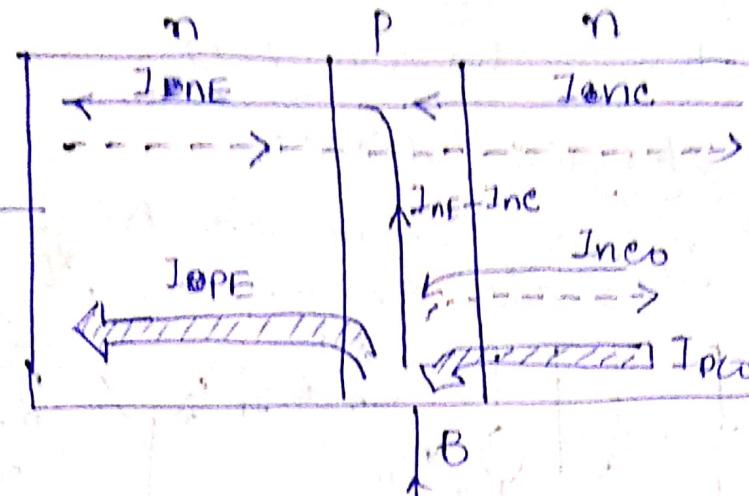

collector junction are collected by the collector and give rise to the current component  $I_{ne}$ .


The difference  $I_{ne} - I_{pc}$  constitutes a part of base current. Since the collector junction is reverse biased there is also reverse saturation current through the junction. This component is denoted by  $I_{co}$ . It consists of two parts:  $I_{nc}$ , due to movement of minority electrons from base to collector, and  $I_{po}$ , due to movement of minority holes from collector to base.

So,  $I_{co} = I_{pc} + I_{nc}$ . So total collector current is  $I_c = I_{ne} + I_{co}$ .


and  $I_E = I_B + I_c$ .
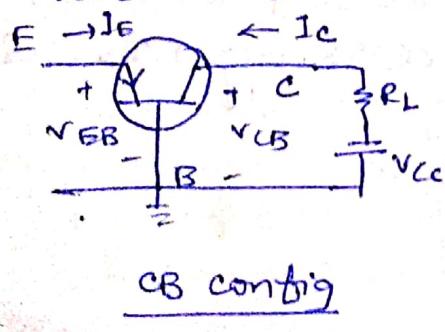
### Mode of transistor operation :-


A transistor can be operated in any of the following three modes depending on the common terminal between the I/p and O/p terminal.



CE config

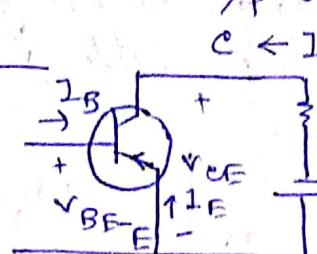

CE config

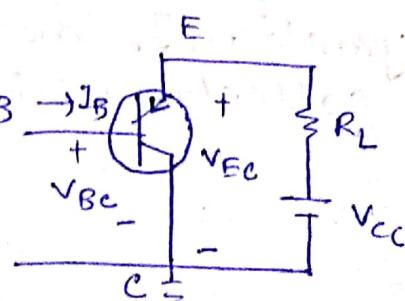


7

## Characteristic curves of a transistor :-

### Common Base characteristics :-

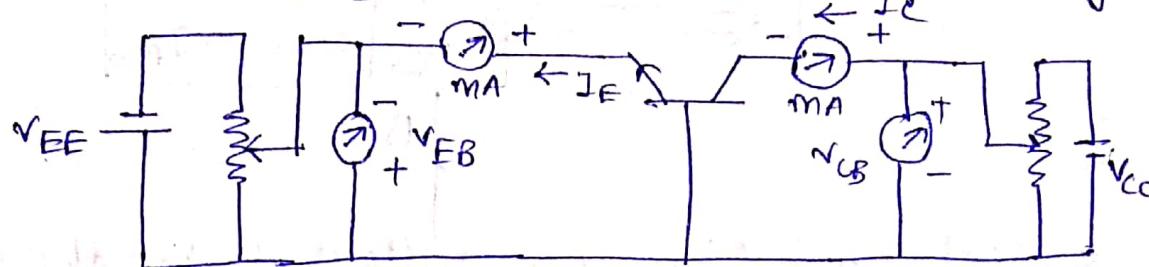
#### a) Input characteristics :-

The circuit arrangement for drawing the CB static characteristic curves as shown in fig



#### a) Input characteristics :-

for normal operation, the emitter base junction is biased in forward direction. Therefore, the variation of  $I_E$  with  $V_{EB}$  with fixed  $V_{CB}$  is similar to the forward characteristic of a P-n diode. However, with an increase of  $|V_{CB}|$ ,  $I_E$  increases for a fixed  $V_{EB}$ . When  $|V_{CB}|$  increases, the width of the depletion region at the collector junction increases, thereby reducing the effective base width. The change of effective base width by the collector voltage is known as the Early effect. The decrease of the effective base width enhances the concentration gradient of holes in the base region. Since the hole current injected across the emitter junction is proportional to the hole concentration gradient at that junction,  $I_E$  increases with increasing reverse collector voltage.

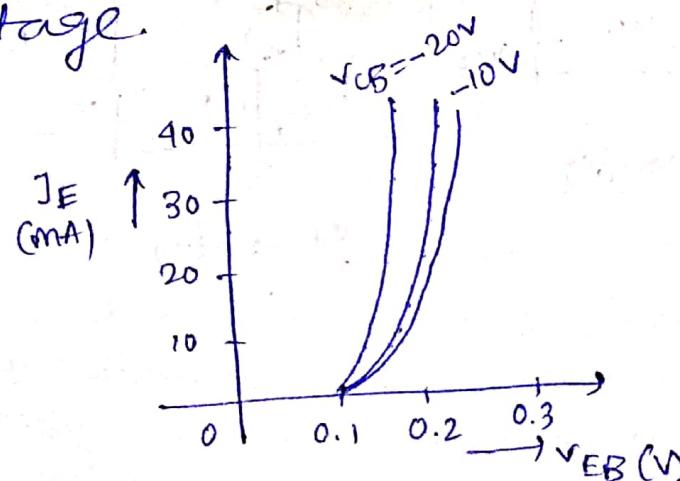


## b) Output Characteristics :-

for the CB mode, the collector current  $I_C$  is the o/p current, the collector-base voltage  $V_{CB}$  is the o/p voltage and emitter current  $I_E$  is the i/p current. So, the plot of  $I_C$  vs  $V_{CB}$  with  $I_E$  as a parameter is the CB o/p characteristic. The o/p characteristics can be divided into three distinct regions, namely, the active region, the saturation region and the cut-off region.

In active region transistor used as an amplifier. In this region, the emitter junction is forward biased and collector junction is reverse biased. When the emitter junction is forward biased, an emitter current  $I_E$  flows. Since the recombination in the base region is small, most of the current will reach the collector. However  $|I_C|$  rises slightly with an increase of  $|V_{CB}|$ . and o/p characteristics are nearly parallel lines.

In saturation region, both emitter & collector junctions are forward biased. In fig. it represents the region to the left of the ordinate  $V_{CB} = 0$  and above the characteristic for  $I_E = 0$ . It is seen that  $I_C$  is not zero even when  $V_{CB} = 0$ . This happens so because the injected carriers still find a potential down at the collector junction due to contact potential difference. To reduce  $I_C$  to zero it is necessary to apply a small forward bias to the collector and this causes the collector current exponentially with collector base forward

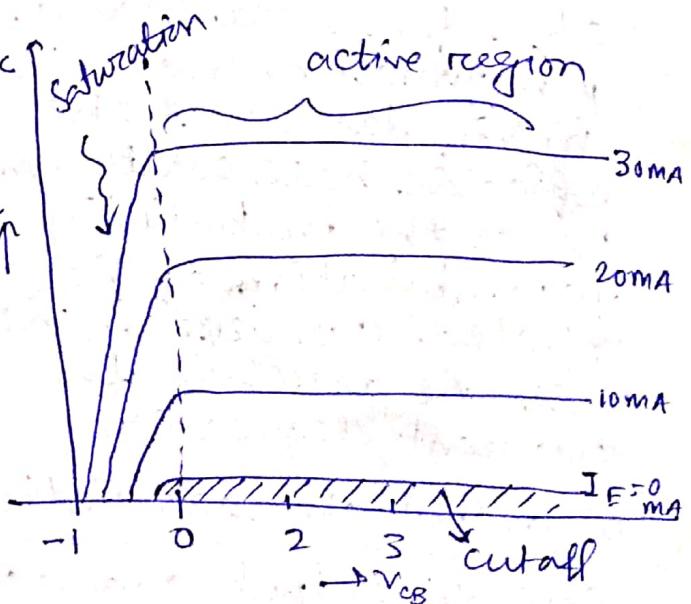


Scanned with CamScanner

⑨ voltage as in a p-n diode. The large change in the collector current for a small change in  $V_{CB}$  in the saturation region is thus accounted for.

~~ce~~ In cut-off region both the emitter and collector junctions are reverse biased. In fig this region is located to the right of the ordinate  $V_{CB} = 0$  and below the characteristic for  $I_E = 0$
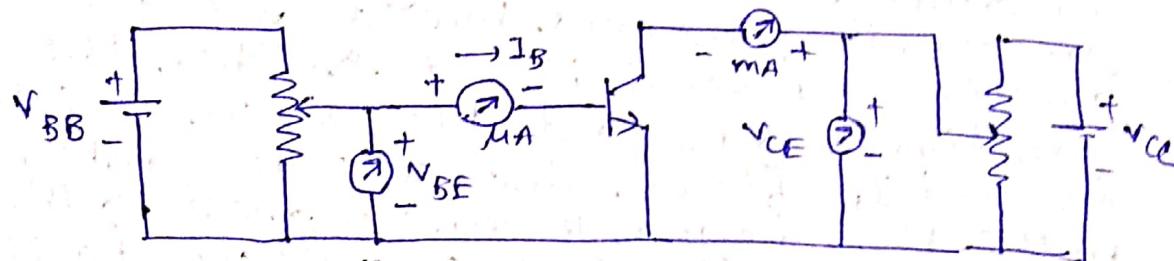
### Common Emitter characteristics :-

The circuit arrangement for drawing the CE characteristics of the most prevalent n-p-n transistor is shown in fig. below -



### a) Input characteristics :-

The variation of the i/p base current ( $I_B$ ) with i/p base emitter voltage  $V_{BE}$  taking the o/p collector emitter voltage  $V_{CE}$  as parameter, gives the CE input characteristics as shown in fig

The ce characteristics

are similar to that

of a forward biased

p-n junction. Increase

in  $V_{CE}$  decreases the

effective base width and


hence the probability of

recombination of the

injected carriers in the

base. As a result the recombination base


current decreases,

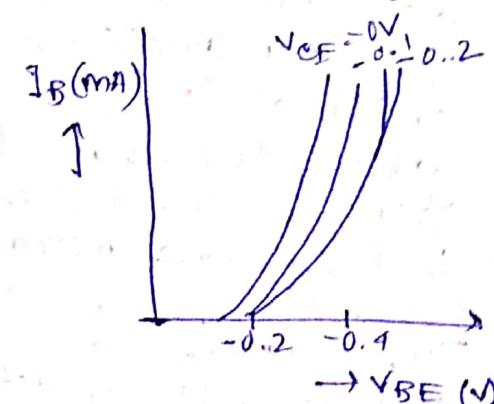

### b) output characteristics :-

The CE output characteristics are obtained by plotting output current  $I_C$  as a function of the o/p voltage  $V_{CE}$  taking i/p base current  $I_B$  as parameter as shown in fig. here the curve may be divided into three regions -

active, cut off and saturation regions.

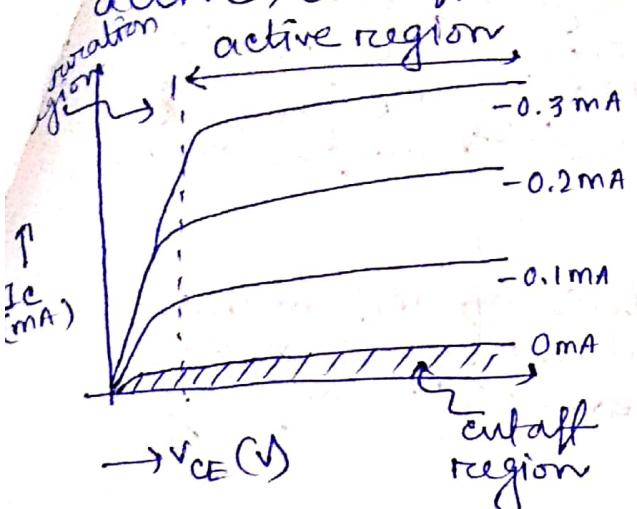

is operated in the active region. The curves in the active region are not horizontal lines.

In CE configuration, the collector current is not cut off when  $I_B = 0$ . To cut off the transistor, in addition to reducing  $I_B$  to zero, the emitter junction has to be reverse biased slightly.

In this region, both the collector and emitter junctions are forward biased by at least the cut-in voltage. Since the voltage  $|V_{EB}|$  or  $|V_{CB}|$  for a forward biased junction is only a few tenths of a volt and  $V_{CE} = V_{CB} - V_{EB}$ , we find that  $V_{CE}$  is also a few tenths of a volt at saturation. So, the saturation region lies very close to the zero voltage axis, when all the curves coincide and fall quickly towards the origin.

What is  $\alpha$  and  $\beta$  of a transistor:-

The quantity  $\alpha$  represents the fraction of the emitter current contributed by the carriers injected into the base and reaching the collector.  $\alpha$  is called the dc current gain of the common base transistor.

$$\alpha = \frac{I_c}{I_E}$$

$\alpha$  lies between 0.95 and 0.995.  $\alpha$  is not a constant for a given transistor but varies with the emitter current  $I_E$ , collector voltage  $V_{CB}$  and the temperature.

(11)

The maximum current gain of a transistor operated in the common-emitter mode is denoted by  $\beta$ . It is also denoted by  $h_{FE}$ . It is also called forward current transfer ratio.

$$\beta(h_{FE}) = \frac{I_C}{I_B}$$

commercial transistor have value of  $h_{FE}$  in the region from 20 to 200. The value of  $\beta$  is not same for any two transistor even belonging to the same type.

Relation between  $\alpha$  and  $\beta$  :-

we know that,  $I_E = I_C + I_B$

$$\Rightarrow \frac{I_E}{I_C} = 1 + \frac{I_B}{I_C}$$

$$\Rightarrow \frac{1}{\alpha} = 1 + \frac{1}{\beta}$$

$$\Rightarrow \frac{1}{\beta} = \frac{1}{\alpha} - 1$$

$$= \frac{1-\alpha}{\alpha}$$

$$\Rightarrow \boxed{\beta = \frac{\alpha}{1-\alpha}}$$

Establish the relation  $I_C = \beta I_B + (1+\beta) I_{Co}$  :-

we know that,  $I_C = \alpha I_E + I_{Co}$


$$= \alpha(I_B + I_C) + I_{Co}$$

$$\Rightarrow I_C(1-\alpha) = \alpha I_B + I_{Co}$$

$$\Rightarrow I_C = \frac{\alpha}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{Co}$$

$$= \beta I_B + (1+\beta) I_{Co}$$

## Transistor as an amplifier :-

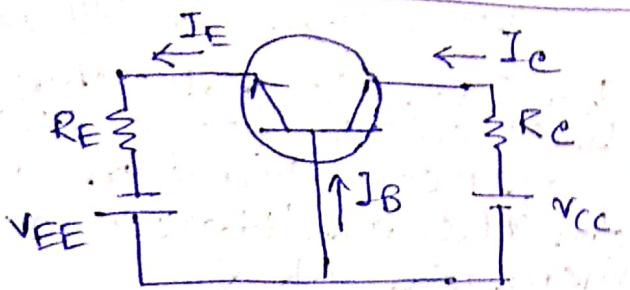

Total power across I/P

$$P_E = I_E^2 R_E$$

Total power across O/P

$$P_C = I_C^2 R_C$$

$$\text{power gain, } A_P = \left| \frac{\text{o/p power}}{\text{i/p power}} \right| = \left| \frac{P_C}{P_E} \right|$$

$$= \frac{I_C^2 R_C}{I_E^2 R_E}$$

$$= \frac{I_C^2 R_C}{(I_B + I_C)^2 R_E}$$

$$= \frac{I_C^2 R_C}{I_C^2 R_E} \quad [\because I_B \ll I_C]$$

$$= \frac{R_C}{R_E}$$

AS,  $R_C \gg R_E$ ,  $\therefore A_P > 1$

Thus a weak signal applied in the I/P circuit appears in the amplified form in the collector circuit. Thus transistors act as an amplifier.

What is punch through?

As the reverse bias of the collector junction is increased, the effective base width decreases (Early effect). At a certain reverse bias of the collector junction, the depletion region covers the base, reducing the effective base width to zero. As the collector voltage penetrates the base, the potential barrier at the emitter junction is lowered. As a result an excessively large emitter current flows. This phenomenon is called punch-through.