
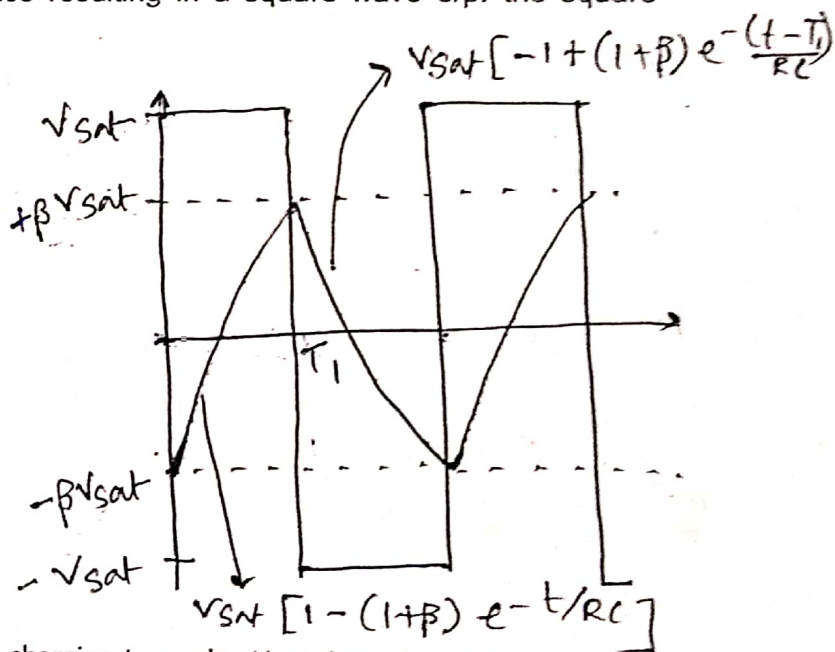


Multivibrator:

Multivibrator is a relaxation oscillator generating nonsinusoidal waveform. There are three classes of multivibrators: astable, bistable & monostable.

Astable multivibrator:

The principal of generation of square wave o/p is to force an opamp to operate in the saturation region. A fraction of o/p voltage is $\beta = R_2/(R_1+R_2)$ of the o/p is feedback to the +ve i/p terminal. Thus the V_{ref} is βV_o & take values as $+\beta V_{sat}$ or $-\beta V_{sat}$. The o/p is also feedback to the -ve i/p terminal after integrating by means of a lowpass RC combination whenever i/p at the -ve terminal just exceeds V_{ref} switching takes place resulting in a square wave o/p. the square wave generator is called astable multivibrator.

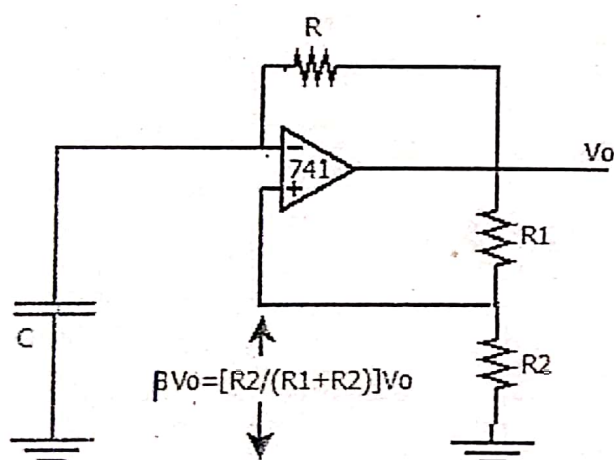

When the o/p is a $+V_{sat}$, the capacitor now starts charging towards $+V_{sat}$ through resistance R . The voltage at the +ve i/p terminal is held at $+\beta V_{sat}$ by R_1 & R_2 combination. This condition continues as the charge on C rises, until it has just exceeded $+\beta V_{sat}$, when the voltage just greater than this reference voltage, the o/p is driven to $-V_{sat}$. At this instant, the capacitor starts to discharge through R towards $-V_{sat}$. When the o/p voltage switches to $-V_{sat}$, the capacitor charge more & more negatively until its voltage just exceeds $-\beta V_{sat}$. The cycle is repeated itself.

The voltage across the capacitor as a function of time is given by, $V_c = V_f + (V_i - V_f)e^{-t/RC}$

The final value $V_f = +V_{sat}$, Initial value = $-\beta V_{sat}$

$$V_c = V_{sat} + (-\beta V_{sat} - V_{sat})e^{-t/RC}$$

$$= V_{sat} - V_{sat}(1+\beta)e^{-t/RC}$$

At $t=T_1$, voltage across capacitor reaches βV_{sat}

$$\text{So, } V_c = \beta V_{sat} = V_{sat} - V_{sat}(1+\beta)e^{-T_1/RC}$$


$$T_1 = RC \ln(1+\beta)/(1-\beta)$$

Total time period,


$$T = 2T_1 = 2RC \ln(1+\beta)/(1-\beta)$$

Monostable multivibrator:

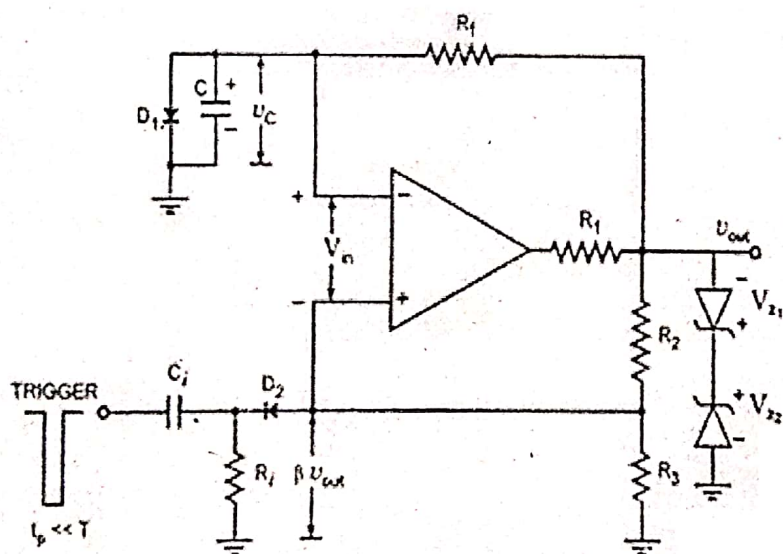
Monostable multivibrator has one stable ^{state} state & other is quasistable state. The ckt is useful for generating signal o/p pulse of adjusting signal o/p pulse of adjustable time duration in response to a trigger signal.




(a) Basic Circuit

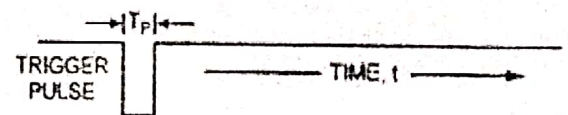

(b) Negative Trigger Pulse

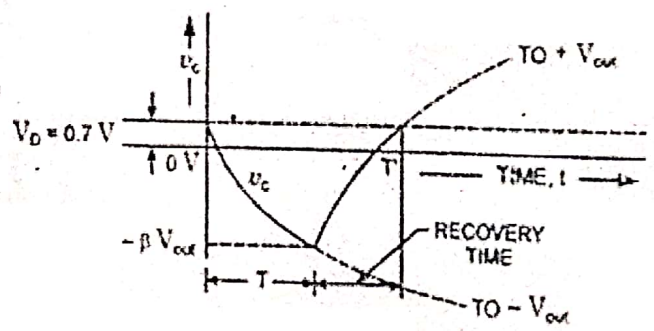

(c) Waveform of v_c

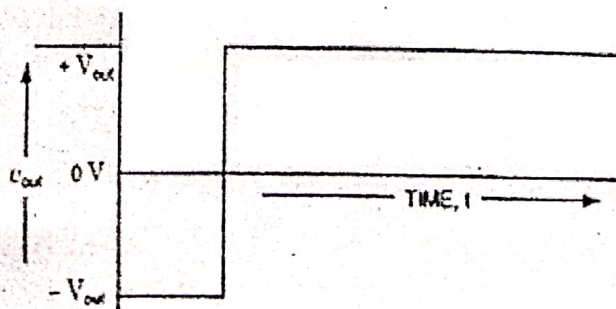

(d) Output Waveform

A diode D_1 clamps the capacitor voltage to 0.7V when the o/p is at $+V_{\text{sat}}$. A negative going pulse signal of magnitude V_1 passing through the differentiator R_1C_1 & diode D_2 produces a negative going triggering impulse & is applied to the +ve i/p terminal. In stable state, the o/p V_0 is $+V_{\text{sat}}$. The diode D_1 conducts & V_c the voltage across the capacitor C gets clamped to $+0.7\text{V}$. The voltage at the +ve i/p terminal through R_1R_2 is $+\beta V_{\text{sat}}$. Now, if a negative trigger of magnitude V_1 is applied to the +ve i/p terminal, the o/p of opamp will switch from $+V_{\text{sat}}$ to $-V_{\text{sat}}$. The diode will now get reverse biased & the capacitor gets charge exponentially to $-V_{\text{sat}}$ through resistance R . The voltage at the +ve i/p terminal is now $-\beta V_{\text{sat}}$. When the capacitor voltage V_c becomes just slightly negative than $-\beta V_{\text{sat}}$. The capacitor C now starts charging to $+V_{\text{sat}}$ through R until V_c is 0.7V .

The o/p voltage, $V_0 = V_f + (V_i - V_f) e^{-t/RC}$

Where $V_f = \text{final value} = -V_{\text{sat}}$

$V_i = \text{initial value} = V_D$ (diode forward voltage)

The o/p V_c is, $V_c = -V_{\text{sat}} + (V_D + V_{\text{sat}}) e^{-t/RC}$

At $t=T$, $V_c = -\beta V_{\text{sat}}$

$-\beta V_{\text{sat}} = -V_{\text{sat}} + (V_D + V_{\text{sat}}) e^{-t/RC}$

Or, $V_{\text{sat}}(1-\beta) = V_{\text{sat}}(1+V_D/V_{\text{sat}}) e^{-t/RC}$

Or, $(1-\beta) = (1+V_D/V_{\text{sat}}) e^{-t/RC}$


Or, $e^{-t/RC} = (1-\beta) / (1+V_D/V_{\text{sat}})$

Or, $t/RC = \ln(1+V_D/V_{\text{sat}}) / (1-\beta)$

At $t=T$, $T = RC \ln(1+V_D/V_{\text{sat}}) / (1-\beta)$


Bistable multivibrator:

An incoming waveform is converted into short pulses and these are used to trigger the operational amplifier to change between its two saturation states. To prevent small levels of noise triggering the circuit, hysteresis is introduced into the circuit, the level being dependent upon the application required. A fraction $\beta = R_3/(R_2+R_3)$ of the o/p is feedback to the +ve i/p terminal. A RC combination is used in -ve i/p terminal.

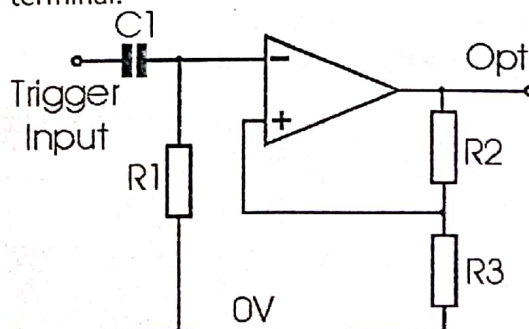

Bistable multivibrator operational amplifier circuit

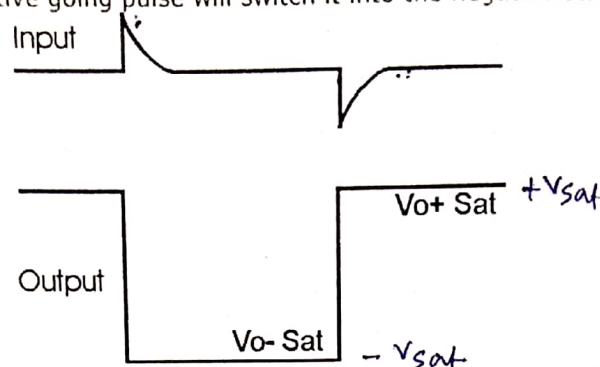The bistable circuit has two stable states. These are the positive and negative saturation voltages of the operational amplifier operating with the given supply voltages. The circuit can then be switched between them by applying pulses. A negative going pulse will switch the circuit into the positive saturation voltage, and a positive going pulse will switch it into the negative state.



Waveforms for the bistable multivibrator operational amplifier circuit

It is very easy to calculate the points at which the circuit will trigger. The positive going pulses need to be greater than V_{o-Sat} through the potential divider, i.e. $V_{o-Sat} \times R_3 / (R_2 + R_3)$, and similarly the negative going pulses will need to be greater than V_{o+Sat} through the potential divider, i.e. $V_{o+Sat} \times R_3 / (R_2 + R_3)$. If they are not sufficiently large then the bistable will not change state.

What are the basic difference between Astable, monostable and bistable multivibrator?

→ i) An astable multivibrator has no stable state but only two quasi-stable states which it keeps on oscillating automatically at a rate determined by the circuit component.

Monostable multivibrator has one stable state and one quasi-stable state. The circuit remains in the stable state until a triggering pulse causes a transition to the quasi-stable state. Then after some time it returns automatically to its stable state.

Bistable multivibrator has two stable states. The circuit remains in one of these stable states until a triggering signal causes transition to the other stable state.

ii) An astable multivibrator is also called free-running multivibrator that produces a square wave pulses at a fixed frequency. A monostable multivibrator is also called one-shot multivibrator.

Bi Monostable multivibrator is called flipflop that produces a single pulse that produces a single pulse either positive or [4] negative