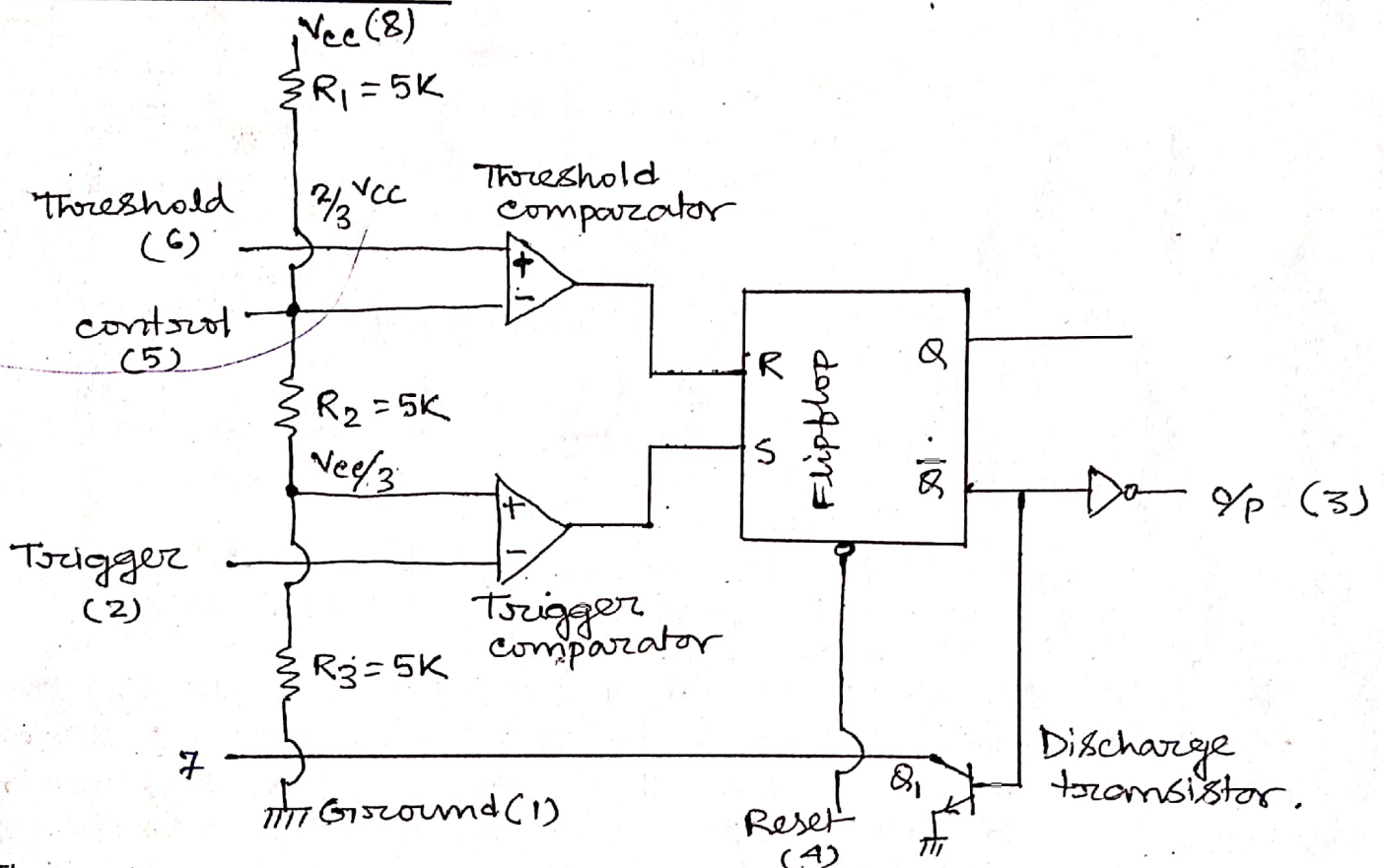


Architecture of 555 timer:

There are two case:


1) The threshold comparator o/p is high when the threshold pin (pin 6) goes above  $2V_{cc}/3$  & 2) the trigger comparator o/p is high when the trigger pin (pin 2) goes below  $V_{cc}/3$ .

Case 1: when the voltage at pin 6 exceeds  $2V_{cc}/3$ , the o/p of the threshold comparator jumps high, which resets the Flip Flop i.e.  $\overline{Q}$  high & the o/p of the <sup>timer</sup> ~~opamp~~ become low. When  $\overline{Q}$  is high, the internal NPN transistor  $Q_1$  goes into saturation & the discharge pin (pin 7) is pulled down near to the ground by this saturated transistor.

Case 2: When the voltage at pin 2 goes below  $V_{cc}/3$ , then the trigger comparator o/p jumps high which sets the Flip Flop i.e.  $\overline{Q}$  is low & o/p of the timer become high. For low o/p at  $\overline{Q}$  the transistor  $Q_1$  is cutoff & the discharge pin (pin 7) can not pass any current through the transistor  $Q_1$  i.e. pin 7 is virtually disconnected.

If pin 4 is made low then  $\overline{Q}$  o/p of the RS flipflop becomes high & o/p becomes low. If the reset pin is not used, then this pin should be made inactive by connecting this to a power supply.

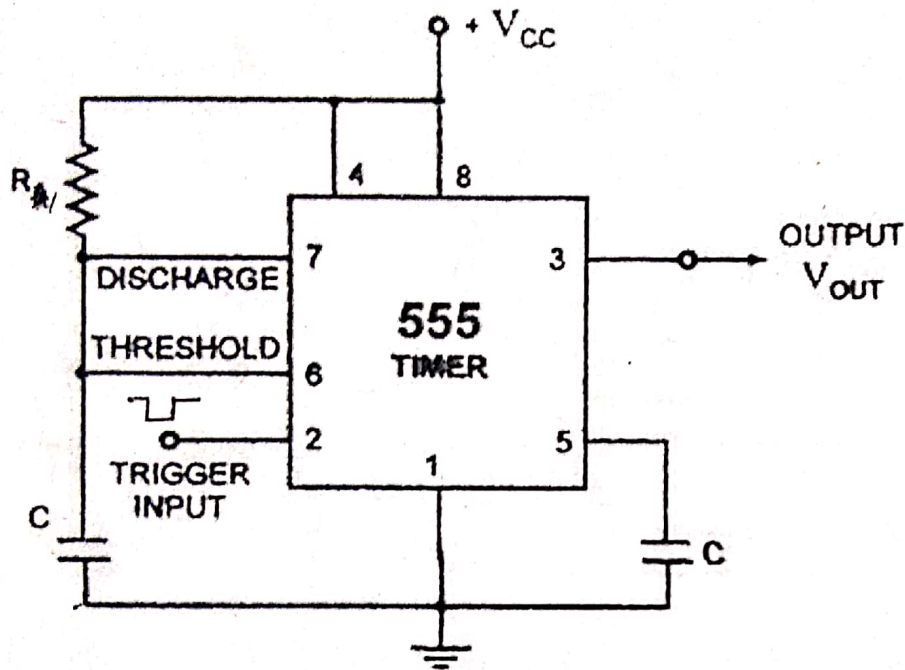
### Monostable multivibrator using 555 timer:



*Circuit of The Timer 555  
as a Monostable Multivibrator*


**Stable state:** In fig. show a monostable multivibrator when the power is switched on before any trigger input, the capacitor  $C$  will try to be charged toward  $V_{CC}$  through  $R$ , while charging, the capacitor voltage will reach  $2V_{CC}/3$  at the threshold pin (pin 6). This will cause the o/p of the threshold comparator to jump high. This will reset the internal RS flipflop. Therefore  $\overline{Q}=1$  & the o/p (pin 3) will be low because of the inverter is connected to  $\overline{Q}$ . The high o/p of  $\overline{Q}$  will saturate the internal transistor & for this reason the capacitor  $C$  will be fully discharge through the discharge pin (pin 7) & the saturated transistor to the ground. Thus in absence of any trigger the capacitor is completely discharge & the o/p is low. This is the stable state of the circuit.

**Quasi stable state:** when the trigger pin of the timer is forced to go below  $V_{CC}/3$  using a negative going pulse, the trigger comparator o/p will be high which set the flipflop ( $\overline{Q}=0$ ), cut off the internal transistor, discharge pin 7 is practically isolated from the ground & the time o/p jump high. The isolation of the discharge pin will allow the capacitor  $C$  to charge through the external resistor  $R$  toward  $V_{CC}$  with a time const.  $RC$ . The timing diagram is shown below.

 

The capacitor voltage  $V_c(t)$  will reach  $2V_{cc}/3$ , the threshold comparator o/p high & reset the RS flipflop. This marks the time o/p low and again saturated the internal transistor. This saturated transistor is now able to discharge pin 7 to the ground & the ckt goes back to the stable state again.
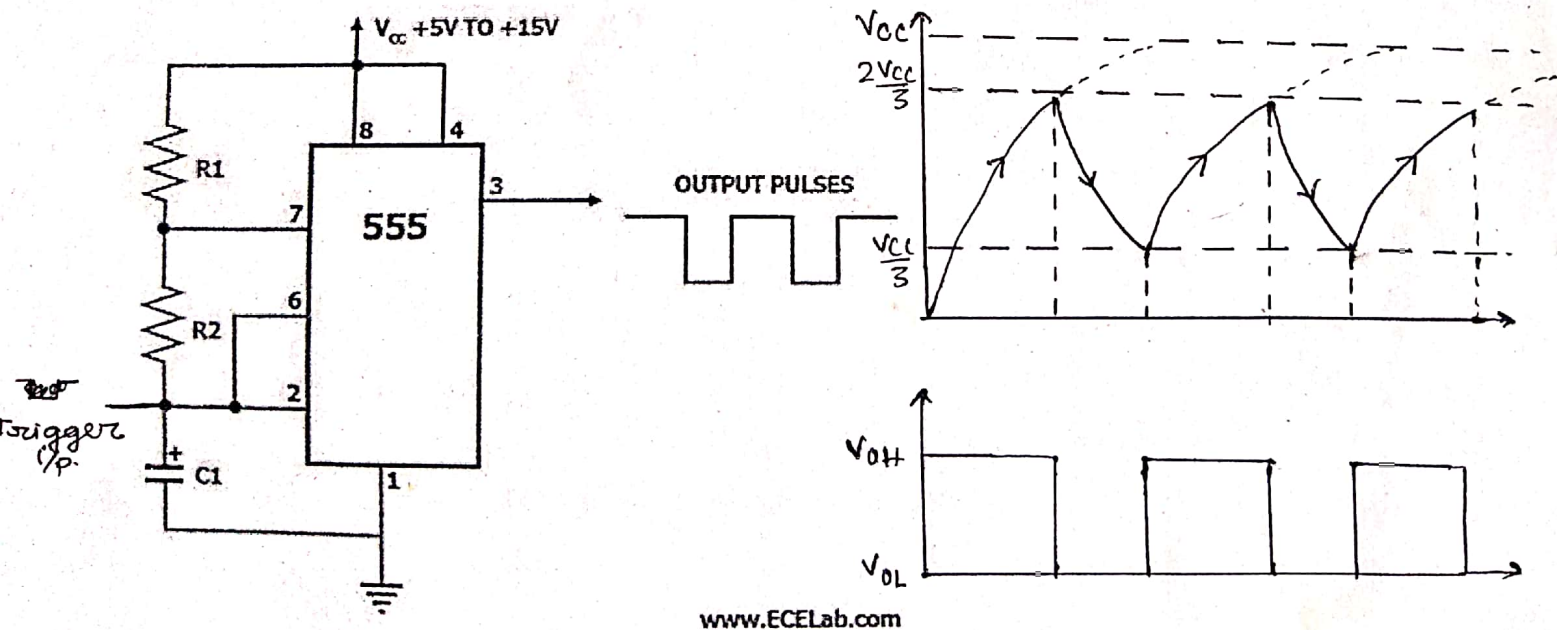
### Astable multivibrator using 555 timer:



www.ECELab.com

When the power supply is switched on the capacitor  $C_1$  acts as a short ckt to ground & the timer is triggered as the capacitor is connected to the trigger pin. So the o/p of the timer becomes high ( $V_{oh}$ ) &



the discharge pin is practically isolated from the ground as the internal transistor of the timer is at cutoff condition because of low  $\overline{Q}$  o/p of the internal RS flipflop. Thus the capacitor begins to charge towards  $V_{cc}$  through the resistor  $R_1$  &  $R_2$  with time const.  $(R_1 + R_2)C$ , but as soon as the capacitor voltage  $V_c(t)$  reaches  $2V_{cc}/3$  the threshold pin (pin 6) sense this voltage & the internal threshold comparator o/p a high voltage which in turn reset the internal RS flipflop of the timer. Thus the  $\overline{Q}$  o/p of this flipflop goes high & o/p at pin 3 goes low. Under this condition the internal transistor goes to saturation & the discharge pin is shorted to ground through the saturated transistor. Now the charged capacitor start to discharge through resistance  $R_2$ . when  $V_c(t)$  at this moment the timer is triggered again. This triggering leads to setting of the internal RS flipflop & so  $\overline{Q}$  becomes low, the o/p of the timer becomes high & the discharge path is cut off. Now the capacitor repeats charging again.