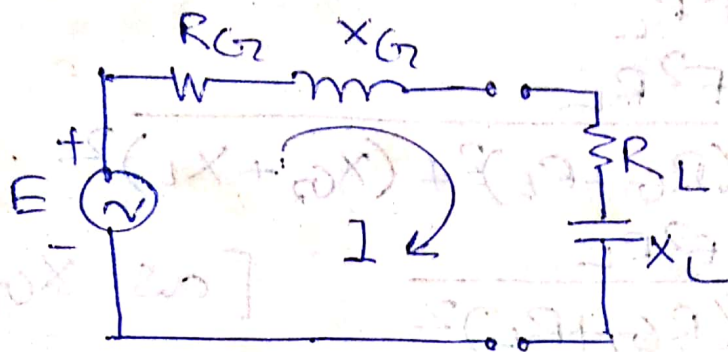


## Maximum power transfer theorem:-

Any two terminal linear network will absorb maximum power from the generator if the load impedance is complex conjugate of the internal impedance of the generator.



Let us consider a circuit with  $Z_G$  and  $Z_L$  are connected in series with the voltage source  $E$ ,  $Z_G$  is the impedance due to generator and  $Z_L$  is the ~~impedance~~ impedance due to load where  $Z_G = R_G + jX_G$  and  $Z_L = R_L + jX_L$

Let  $I$  be the instantaneous current flowing through the circuit, therefore,

$$I = \frac{E}{Z_G + Z_L} = \frac{E}{(R_G + jX_G) + (R_L + jX_L)}$$

$$= \frac{E}{\sqrt{(R_G + R_L)^2 + (X_G + X_L)^2}}$$

Now power absorb by the load,

$$P = I^2 R_L$$

$$= \frac{E^2 R_L}{(R_G + R_L)^2 + (X_G + X_L)^2}$$

$$\Rightarrow \frac{\partial P}{\partial X_L} = \frac{-E^2 R_L \times 2(X_G + X_L)}{[(R_G + R_L)^2 + (X_G + X_L)^2]^2}$$

For  $P = P_{max}$ ,  $\frac{\partial P}{\partial X_L} = 0$

$$\Rightarrow \frac{-E^2 R_L \cdot 2(X_G + X_L)}{[(R_G + R_L)^2 + (X_G + X_L)^2]^2} = 0$$

$$\Rightarrow -2E^2 R_L (X_G + X_L) = 0$$

$$\Rightarrow X_G + X_L = 0$$

$$\Rightarrow X_G = -X_L$$

Again,  $P = I^2 R_L$

$$= \frac{E^2 R_L}{(R_G + R_L)^2 + (X_G + X_L)^2}$$

$$= \frac{E^2 R_L}{(R_G + R_L)^2} \quad [\text{as } X_G = -X_L]$$

$$\Rightarrow \frac{\partial P}{\partial R_L} = \frac{(R_G + R_L)^2 E^2 - E^2 R_L \times 2(R_G + R_L)}{(R_G + R_L)^4}$$

$$= \frac{[(R_G + R_L)^2 - 2R_L(R_G + R_L)] E^2}{(R_G + R_L)^4}$$

$$= \frac{E^2 (R_G + R_L) (R_G + R_L - 2R_L)}{(R_G + R_L)^4}$$

$$= \frac{E^2 (R_G + R_L) (R_G - R_L)}{(R_G + R_L)^4} = \frac{E^2 (R_G - R_L)}{(R_G + R_L)^3}$$



For  $P = P_{\max}$ .

$$\frac{\partial P}{\partial R_L} = 0$$

$$\frac{E^2(R_G - R_L)}{(R_G + R_L)^3} = 0$$

$$\Rightarrow E^2(R_G - R_L) = 0$$

$$\Rightarrow R_G = R_L$$

Hence maximum power Transfer Theorem is proved.

### ✓ Superposition Theorem :-

In a network containing energy source and impedance, the current flowing at any point is the algebraic sum of all current which could be separately flow at that point by energy source.

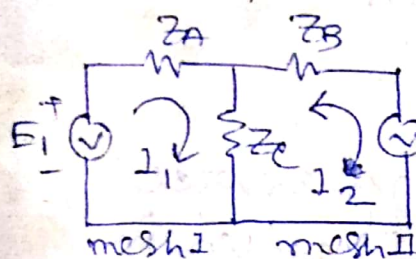


fig ①

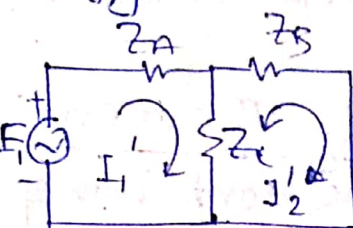


fig ②

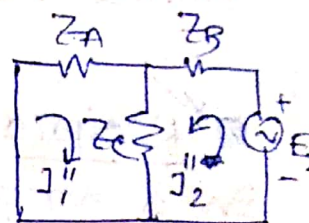


fig ③

Let us consider a ckt consisting of  $Z_A, Z_B, Z_C$  where  $Z_A, Z_B, Z_C$  are impedance and voltage source  $E_1$  and  $E_2$ .

$I_1$  and  $I_2$  be the instantaneous current flowing through mesh I and II.

Now applying KVL we get,

$$E_1 = I_1(Z_A + Z_C) + I_2 Z_C \quad \text{--- ①}$$

$$E_2 = I_2(Z_B + Z_C) + I_1 Z_C \quad \text{--- ②}$$

when  $E_1$  ON and  $E_2$  OFF, then  $I_1'$  and  $I_2'$  are the current flowing through mesh I and II respectively.

$$\text{So, } E_1 = I_1'(Z_A + Z_C) + I_2' Z_C \quad \text{--- ③}$$

$$0 = I_2'(Z_B + Z_C) + I_1' Z_C \quad \text{--- ④}$$



When  $E_1$  'OFF' and  $E_2$  'ON', then  $I_1''$  and  $I_2''$  are the current flowing through mesh I and II respectively.

$$0 = I_1''(Z_A + Z_C) + I_2'' Z_C \quad \text{--- (5)}$$

$$E_2 = I_2''(Z_B + Z_C) + I_1'' Z_C \quad \text{--- (6)}$$

Adding eq. (5) and (6), we get,

$$E_1 = (I_1' + I_1'')(Z_A + Z_C) + (I_2' + I_2'') Z_C \quad \text{--- (7)}$$

$$E_2 = (I_2' + I_2'')(Z_B + Z_C) + (I_1' + I_1'') Z_C \quad \text{--- (8)}$$

comparing eq. (1) with (7) and (2) with (8) we get

$$I_1 = I_1' + I_1''$$

$$I_2 = I_2' + I_2''$$

Hence superposition theorem is proved.

### ✓ Reciprocity Theorem:-

In a network containing energy source and impedance, if an e.m.f is applied in one mesh produces a certain current in the second mesh, then the same e.m.f acting in the second mesh will give an identical current in the first mesh.

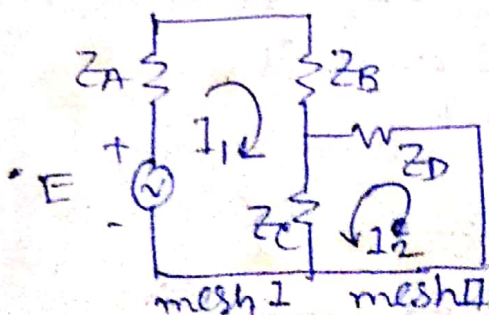


fig ①

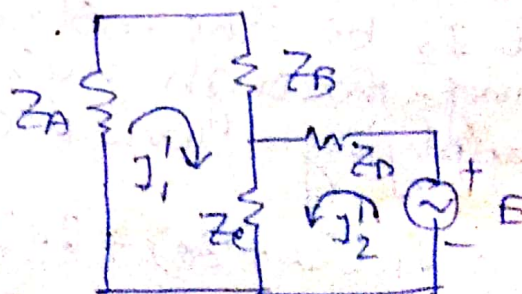


fig ②

Let us consider a circuit with impedance  $Z_A$ ,  $Z_B$ ,  $Z_C$  and  $Z_D$  and a voltage source  $E$ .



$$Z_A + Z_B + Z_C = Z_1 \quad [\text{self impedance of mesh I}]$$

$$Z_C + Z_D = Z_2 \quad [\text{self impedance of mesh II}]$$

$$Z_C = Z_{12} \quad [\text{mutual impedance of mesh I and II}]$$

In fig (1), voltage source  $E$  is connected in mesh I, the current  $I_1$  and  $I_2$  flowing through mesh I and II respectively. Now, applying KVL in fig (1),

$$E = Z_1 I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$0 = Z_2 I_2 + Z_{12} I_1$$

$$= Z_{12} I_1 + Z_2 I_2 \quad \text{--- (2)}$$

using cramer's rule in eq. (1) and (2),

$$I_2 = \frac{\begin{vmatrix} Z_1 & E \\ Z_{12} & 0 \end{vmatrix}}{\begin{vmatrix} Z_1 & Z_{12} \\ Z_{12} & Z_2 \end{vmatrix}} = \frac{-E Z_{12}}{Z_1 Z_2 - (Z_{12})^2}$$

Now voltage source  $E$  is connected in mesh II and current  $I_1'$  and  $I_2'$  flowing through mesh I and II respectively.

Applying KVL in fig (2), we get,

$$E = Z_2 I_2' + Z_{12} I_1' \quad \text{--- (3)}$$

$$0 = Z_1 I_1' + Z_{12} I_2'$$

$$= Z_{12} I_2' + Z_1 I_1' \quad \text{--- (4)}$$

using cramer's rule in eq. (3) and (4),

$$I_1' = \frac{\begin{vmatrix} Z_2 & E \\ Z_{12} & 0 \end{vmatrix}}{\begin{vmatrix} Z_2 & Z_{12} \\ Z_{12} & Z_1 \end{vmatrix}} = \frac{-E Z_{12}}{Z_1 Z_2 - (Z_{12})^2}$$

$$\therefore I_2 = I_1'$$

Hence superposition theorem proved.